

April 18, 2001 - Quiz #2

Name: SOLUTIONS

Recitation: \_\_\_\_\_

problem	grade
1	
2	
3	
4	
5	
total	

**General guidelines** (please read carefully before starting):

- Make sure to write your name on the space designated above.
- **Open book:** you can use any material you wish.
- All answers should be given in the space provided. Please do not turn in any extra material. If you need more space, use the back page.
- You have **120 minutes** to complete your quiz.
- Make reasonable approximations and *state them*, i.e. quasi-neutrality, depletion approximation, etc.
- Partial credit will be given for setting up problems without calculations. **NO** credit will be given for answers without reasons.
- Use the symbols utilized in class for the various physical parameters, i.e.  $\mu_n$ ,  $I_D$ ,  $E$ , etc.
- Every numerical answer must have the proper units next to it. Points will be subtracted for answers without units or with wrong units.
- Use  $\phi = 0$  at  $n_o = p_o = n_i$  as potential reference.
- Use the following fundamental constants and physical parameters for silicon and silicon dioxide at room temperature:

$$n_i = 1 \times 10^{10} \text{ cm}^{-3}$$

$$kT/q = 0.025 \text{ V}$$

$$q = 1.60 \times 10^{-19} \text{ C}$$

$$\epsilon_s = 1.05 \times 10^{-12} \text{ F/cm}$$

$$\epsilon_{ox} = 3.45 \times 10^{-13} \text{ F/cm}$$

(1b) (5 points) We want this inverter to have an average propagation delay  $t_p = 1 \text{ ns}$  when driving a  $C_L = 1 \text{ pF}$  capacitive load. Calculate  $W_n$  and  $W_p$ .

The average propagation delay is:

$$t_p = \frac{1}{2} (t_{PHL} + t_{PLH}) = \frac{1}{2} \left[ \frac{C_L V_{DD}}{\frac{W_n}{L_n} \mu_n C_{ox} (V_{DD} - V_{TN})^2} + \frac{C_L V_{DD}}{\frac{W_p}{L_p} \mu_p C_{ox} (V_{DD} + V_{TP})^2} \right] =$$

$$= \frac{C_L V_{DD} L_n}{2 C_{ox} W_p} \left[ \frac{W_p}{W_n} \cdot \frac{1}{\mu_n (V_{DD} - V_{TN})^2} + \frac{1}{\mu_p (V_{DD} + V_{TP})^2} \right] =$$

Solving for  $W_p$ :

$$W_p = \frac{C_L V_{DD} L_n}{2 C_{ox} t_p} \left[ \frac{W_p}{W_n} \cdot \frac{1}{\mu_n (V_{DD} - V_{TN})^2} + \frac{1}{\mu_p (V_{DD} + V_{TP})^2} \right] =$$

$$= \frac{10^{-12} \times 5 \times 1}{2 \times 3.5 \times 10^{-7} \times 10^{-9}} \left[ 3.6 \frac{1}{400 (5 - 0.5)^2} + \frac{1}{200 (5 - 1)^2} \right] = 5.4 \mu\text{m}$$

where we have used

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-13}}{10 \times 10^{-7}} = 3.5 \times 10^{-2} \text{ F/cm}^2$$

hence

$$W_n = \frac{5.4}{3.6} = 1.5 \mu\text{m}$$

1. (25 points) You are given a CMOS inverter with the following parameters:

$$\begin{array}{lll}
 V_{Tn} = 0.5 \text{ V} & t_{ox} = 10 \text{ nm} & \mu_n = 400 \text{ cm}^2/\text{V} \cdot \text{s} \\
 V_{Tp} = -1 \text{ V} & \lambda_n = \lambda_p = 0.1 \text{ V}^{-1} & \mu_p = 200 \text{ cm}^2/\text{V} \cdot \text{s} \\
 V_{DD} = 5 \text{ V} & L_n = L_p = 1 \text{ } \mu\text{m} & 
 \end{array}$$

(1a) (5 points) Calculate the ratio  $W_p/W_n$  so that  $V_M = 2.5 \text{ V}$ .

$V_M$  is given by:

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_p}{k_n}}}$$

let us solve for  $k_p/k_n$ :

$$\frac{k_p}{k_n} = \left( \frac{V_M - V_{Tn}}{V_{DD} - V_M + V_{Tp}} \right)^2 = \left( \frac{2.5 - 0.5}{5 - 2.5 - 1} \right)^2 = 1.8$$

This ratio is equal to

$$\frac{k_p}{k_n} = \frac{\frac{W_p}{L_p} \mu_p C_{ox}}{\frac{W_n}{L_n} \mu_n C_{ox}} = \frac{W_p \mu_p}{W_n \mu_n}$$

Hence

$$\frac{W_p}{W_n} = \frac{k_p}{k_n} \cdot \frac{\mu_n}{\mu_p} = 1.8 \times 2 = 3.6$$

(1c) (10 points) Estimate  $NM_L$  and  $NM_H$  for this inverter.

We have to start by computing the voltage gain at  $V_M$ :

$$\begin{aligned}
 |A_v| &= (g_{mn} + g_{mp}) (r_{on} \parallel r_{op}) = \frac{g_{mn} + g_{mp}}{\frac{1}{r_{on}} + \frac{1}{r_{op}}} = \frac{g_{mn} + g_{mp}}{g_{on} + g_{op}} \\
 &= \frac{\frac{W_n}{L_n} \mu_n C_{ox} (V_M - V_{in}) + \frac{W_p}{L_p} \mu_p C_{ox} (V_M + V_{TP})}{\frac{W_n}{2L_n} \mu_n C_{ox} (V_M - V_{in})^2 \lambda_n + \frac{W_p}{2L_p} \mu_p C_{ox} (V_M + V_{TP})^2} \\
 &= \frac{2}{\lambda_n} \frac{(V_M - V_{in}) + \frac{W_p}{W_n} \frac{\mu_p}{\mu_n} (V_M + V_{TP})}{(V_M - V_{in})^2 + \frac{W_p}{W_n} \frac{\mu_p}{\mu_n} (V_M + V_{TP})^2} = \frac{2}{0.1} \frac{(2.5 - 0.5) + 1.8 \cdot (2.5 - 1)}{(2.5 - 0.5)^2 + 1.8 (2.5 - 1)^2} = 11.7
 \end{aligned}$$

We now use the standard formulas for  $NM_L$  and  $NM_H$ :

$$NM_L = V_M - \frac{V_{DD} - V_M}{|A_v|} = 2.5 - \frac{5 - 2.5}{11.7} = 2.3 \text{ V}$$


$$NM_H = V_{DD} - V_M \left(1 + \frac{1}{|A_v|}\right) = 5 - 2.5 \left(1 + \frac{1}{11.7}\right) = 2.3 \text{ V}$$

Here is a much faster way to compute the voltage gain:


$$\begin{aligned}
 |A_v| &= \frac{g_{mn} + g_{mp}}{g_{on} + g_{op}} = \frac{\sqrt{2 \frac{W_n}{L_n} \mu_n C_{ox} \bar{I}_D} + \sqrt{2 \frac{W_p}{L_p} \mu_p C_{ox} \bar{I}_D}}{\lambda_n \bar{I}_D + \lambda_p \bar{I}_D} = \frac{\sqrt{2} \sqrt{\frac{W_n}{L_n} \mu_n C_{ox}} + \sqrt{\frac{W_p}{L_p} \mu_p C_{ox}}}{2\lambda} \\
 &= \frac{1}{\lambda} \frac{\sqrt{1 + \frac{k_p}{k_n}}}{V_M - V_{in}}
 \end{aligned}$$

where we have used the fact that  $\bar{I}_{Dn} = -\bar{I}_{Dp} = \bar{I}_D$  and  $\lambda_n = \lambda_p = \lambda$ .

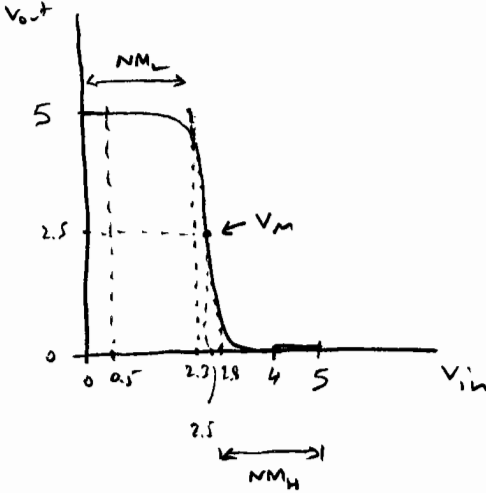(1d) (5 points) Sketch and appropriately label the voltage transfer characteristics of this inverter.



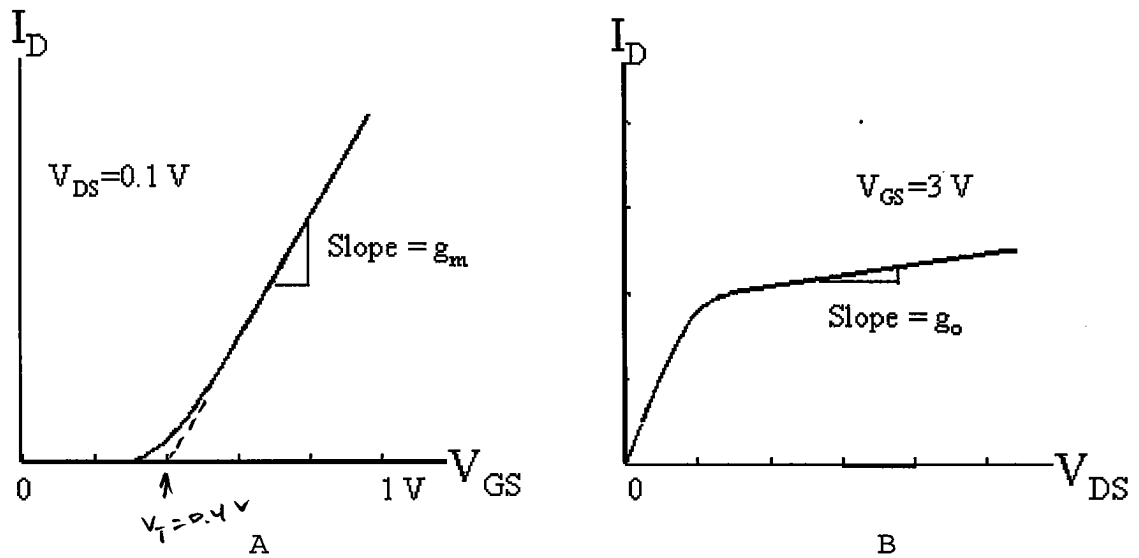2. (20 points) You are given the following I-V characteristics for a n-MOSFET with  $t_{ox} = 10 \text{ nm}$ ,  $W = 10 \mu\text{m}$ , and  $L = 1 \mu\text{m}$ . The gate material is  $n^+$ -doped polysilicon. The body is tied up to the source.



In (A),  $g_m = 1.4 \times 10^{-4} \text{ A/V}$ . In (B),  $g_o = 5.7 \times 10^{-5} \text{ A/V}$ .

(2a) (5 points) From (A), estimate the threshold voltage,  $V_T$ .

From (A), by simple extrapolation we get:

$$V_T \approx 0.4 \text{ V}$$

(2b) (5 points) From (A), estimate the electron mobility,  $\mu_n$ .

In (A) the transistor is biased in the linear regime ( $V_{DS}$  is small).

The transistor current is given by:

$$I = \frac{W}{L} \mu_n C_{ox} \left( V_{GS} - \frac{V_{DS}}{2} - V_T \right) V_{DS}$$

The transconductance is then:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{W}{L} \mu_n C_{ox} V_{DS}$$

Solving for  $\mu_n$ :

$$\mu_n = \frac{g_m L}{W C_{ox} V_{DS}} = \frac{1.4 \times 10^{-4} \times 10^{-4}}{10 \times 10^{-4} \times 3.45 \times 10^{-7} \times 0.1} = 406 \text{ cm}^2/\text{V}\cdot\text{s}$$

with

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-13}}{10 \times 10^{-7}} = 3.45 \times 10^{-7} \text{ F/cm}^2$$

(2d) (5 points) Estimate the saturation voltage,  $V_{DSsat}$ , and the saturation current,  $I_{Dsat}$ , corresponding to the characteristics in (B).

In a MOSFET:

$$V_{Dsat} = V_{GS} - V_T$$

Hence, for the data in (B):

$$V_{Dsat} = 3 - 0.4 = 2.6 \text{ V.}$$

$I_{Dsat}$  is simply:

$$\bar{I}_D = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2 = \frac{10}{2 \times 1} 406 \times 3.45 \times 10^{-7} (3 - 0.4)^2 = 4.7 \text{ mA}$$

(2e) (5 points) From (B), estimate the width of the channel pinch-off region,  $\Delta L$ , at  $V_{DS} = 4 \text{ V}$ .

To the first order we know that

$$g_0 = \lambda \bar{I}_D = \frac{\Delta L}{L} \frac{\bar{I}_D}{V_{DS} - V_{Dsat}}$$


Solving for  $\Delta L$ :

$$\begin{aligned} \Delta L &= \frac{g_0 L (V_{DS} - V_{Dsat})}{\bar{I}_D} = \frac{5.7 \times 10^{-5} \times 10^{-4} (4 - 2.6)}{4.7 \times 10^{-3}} = 1.7 \times 10^{-6} \text{ cm} \\ &= 0.017 \mu\text{m} \end{aligned}$$

or 1.7% of the channel length (pretty small).



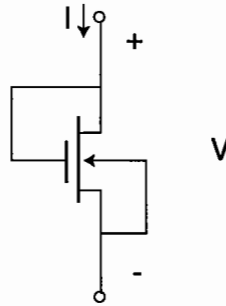3. (20 points) An n-channel MOSFET is wired up in the form indicated below. This is an enhancement-mode device ( $V_T > 0$ ). Neglect channel length modulation.




(3a) (10 points) In terms of usual MOSFET parameters, derive suitable equations for the I-V characteristics of the resulting two-terminal device. Sketch the I-V characteristics in a linear scale.

For  $V > V_T$ , the MOSFET is in the saturation regime since  $V_{GD} = 0 < V_T$ .  
The I-V characteristics are then:

$$I = \frac{W}{2L} \mu_n C_{ox} (V - V_T)^2$$

For  $V < V_T$ , the MOSFET is cut-off and  $I = 0$


The I-V characteristics then look like:

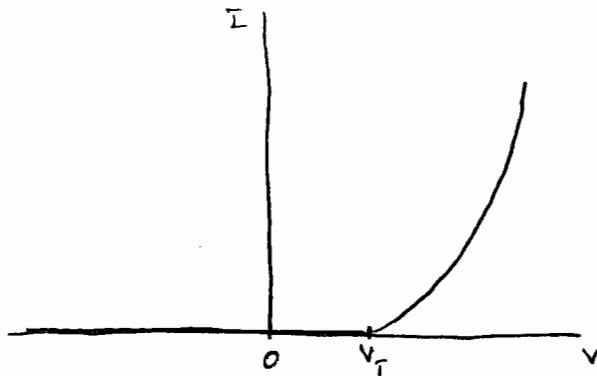


This looks pretty much like a diode except that the forward current branch is quadratic rather than exponential.

(3b) (10 points) Sketch a complete high-frequency small-signal equivalent circuit model for this two-terminal device for situations in which  $V > V_T$ . Express all small-signal elements in terms of those of the MOSFET, i.e.: as a function of  $g_m$ ,  $g_o$ ,  $C_{gs}$ ,  $C_{gd}$ ,  $C_{sb}$ , etc.

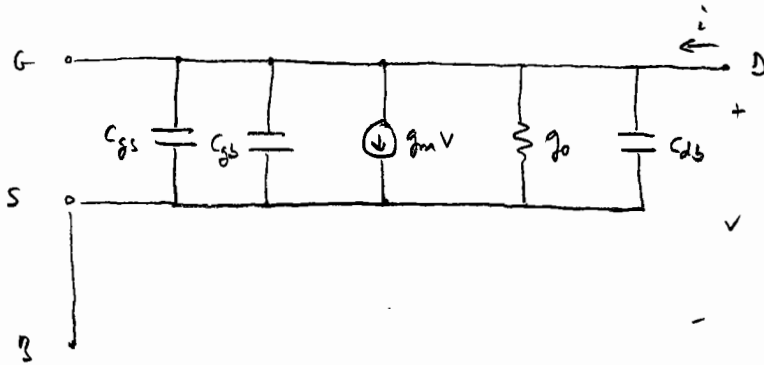
if we look at the small-signal equivalent circuit model of a MOSFET in saturation (appropriate in this case for  $v > v_T$ ), we see that it gets simplified because the body is shorted to the source and the gate is shorted to the drain. That effectively kills  $C_{sb}$ ,  $g_{mb}$  and  $C_{gd}$ . we are then left with:



This can be simplified to:

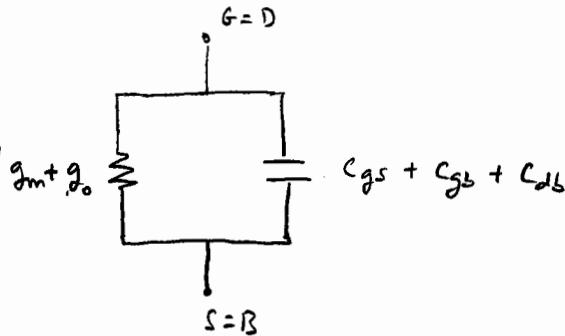

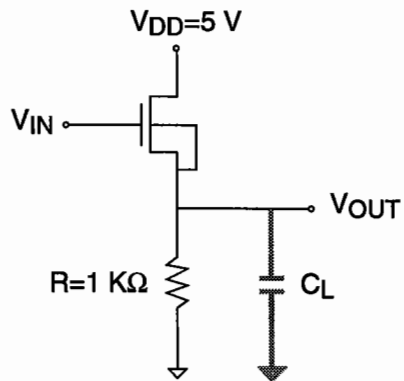4. (15 points) An NMOS inverter with a resistor pull up was miswired and ended up as sketched below.



The parameters of the transistor are:  $\mu_n C_{ox} = 50\ \mu\text{A}/\text{V}^2$ ,  $W/L = 5$ , and  $V_T = 1\text{ V}$ . Neglect channel length modulation in this problem.

(4a) (5 points) For  $V_{IN} = 0$ , in what regime is the transistor biased? How much is  $V_{OUT}$ ? (numerical answer expected).

For  $V_{IN} = 0$  the transistor is cut-off, as a result, no current flows through the resistor and  $V_{OUT} = 0$ .

(4b) (10 points) For  $V_{IN} = 5\text{ V}$ , in what regime is the transistor biased? How much is  $V_{OUT}$ ? (you can leave the result in the form of an equation where  $V_{OUT}$  is the only unknown).

For  $V_{IN} = 5\text{ V}$ , the transistor is in saturation since  $V_{DS} = 0\text{ V} (< V_T)$ .

The current flowing through the transistor is

$$\begin{aligned} \bar{I}_D &= \frac{K}{2} (V_{IN} - V_{OUT} - V_T)^2 = \frac{5}{2} 50 \times 10^{-6} (5 - V_{OUT} - 1)^2 \\ &= 1.25 \times 10^{-4} (4 - V_{OUT})^2 \end{aligned}$$

The current flowing through the resistor is

$$\bar{I}_R = \frac{V_{OUT}}{R} = 10^{-3} V_{OUT}$$

Since  $\bar{I}_R = \bar{I}_D$ , we have

$$1.25 \times 10^{-4} (4 - V_{OUT})^2 = 10^{-3} V_{OUT}$$

or

$$1.25 \times 10^{-4} V_{OUT}^2 - 2 \times 10^{-3} V_{OUT} + 2 \times 10^{-3} = 0$$

or

$$V_{OUT}^2 - 16 V_{OUT} + 16 = 0$$

The solution is:

$$V_{OUT} \approx 1.1\text{ V}$$

5. (20 points) In a certain pn junction diode at room temperature at a particular forward bias voltage, the current supported by hole injection into the n-side of the diode is  $100 \mu\text{A}$ .

The quasi-neutral width of the n-side of the diode is  $w_n - x_n = 1 \mu\text{m}$ . The hole diffusion coefficient is  $10 \text{ cm}^2/\text{s}$ . The pn junction area is  $10 \mu\text{m}^2$ .

Make and state suitable approximations.

(5a) (5 points) Estimate the hole concentration at the space-charge region edge of the n quasi-neutral region. (numerical answer expected).

The current is given by:

$$I_p = q A D_p \frac{p(x_n)}{w_n - x_n}$$

Solving for  $p(x_n)$ :

$$p(x_n) = \frac{I_p (w_n - x_n)}{q A D_p} = \frac{100 \times 10^{-6} \times 10^{-4}}{1.6 \times 10^{-19} \times 10 \times 10^{-8} \times 10} = 6.3 \times 10^{16} \text{ cm}^{-3}$$

(5b) (5 points) Estimate the velocity at which holes are injected at the edge of the n quasi-neutral region (numerical answer expected).

At the edge of the quasi-neutral region we can write:

$$I_p = q A p(x_n) v_p(x_n)$$

Solving for  $v_p(x_n)$ :

$$v_p(x_n) = \frac{I_p}{q A p(x_n)} = \frac{100 \times 10^{-6}}{1.6 \times 10^{-19} \times 10^{-7} \times 6.3 \times 10^{16}} = 10^5 \text{ cm/s}$$

(5c) (5 points) Estimate the hole flux arriving at the surface of the n quasi-neutral region. (numerical answer expected).

The hole flux arriving at the surface of the n quasi-neutral region is the same one that was injected at its edge with the space-charge region. This is because all holes that are injected reach the surface.

Hence

$$F_p(w_n) = F_p(x_n) = \frac{I_p}{Aq} = \frac{100 \times 10^{-6}}{10^{-7} \times 1.6 \times 10^{-19}} = 6.3 \times 10^{21} \text{ cm}^{-2} \text{ s}^{-1}$$

(5d) (5 points) Estimate the diffusion capacitance associated with hole storage in the n quasi-neutral region. (numerical answer expected).

The hole charge stored in the n-QNR is:

$$Q_p = \tau_p \bar{I}_p = \frac{(w_n - x_n)^2}{2D_p} \bar{I}_p = \frac{(10^{-4})^2}{2 \times 10} \times 100 \times 10^{-6} = 5 \times 10^{-14} \text{ C}$$

The diffusion capacitance is:

$$C_p = \frac{q}{kT} Q_p = \frac{5 \times 10^{-14}}{0.025} = 2 \times 10^{-12} \text{ F}$$