


Massachusetts institute of Technology
Department of Nuclear Science and Engineering
Department of Electrical Engineering and Computer Science

22.071, 6.071 - Introduction to Electronics, Signals and Measurement
Spring 2006

Homework 3
 Due 3/1/06


Problem 1.

Find the currents i_1 and i_2 for the following circuit. What is the magnitude and direction of the current flowing through the 30Ω resistor?

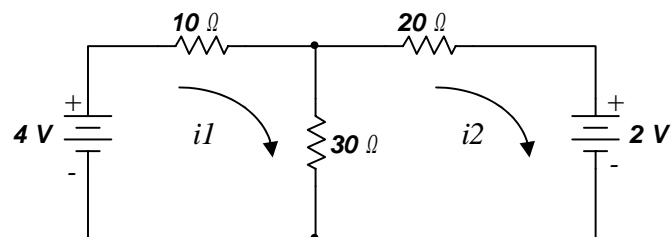


Problem 2.

Using nodal analysis derive and put in a matrix form the equations for the node voltages of the circuit

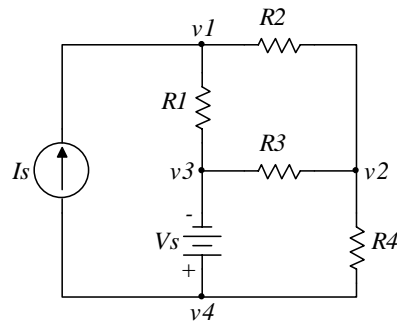

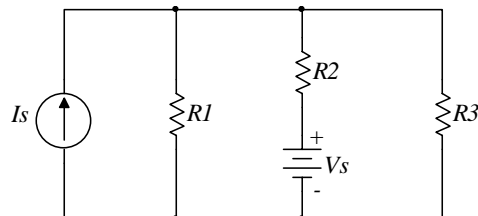Problem 3.

Using the principle of superposition, calculate the current through resistor R_3 .



For the same circuit, calculate the Thevenin equivalent resistance seen by resistor R_3 . Also find the Thevenin voltage and the Norton current seen by load R_3 .

Problem 4.

For the Wheatstone bridge circuit determine the Thevenin equivalent circuit seen by resistor R_L .

