

MITOPENCOURSEWARE
MASSACHUSETTS INSTITUTE OF TECHNOLOGY

6.976

High Speed Communication Circuits and Systems

Lecture 5

High Speed, Broadband Amplifiers


Michael Perrott

Massachusetts Institute of Technology

Copyright © 2003 by Michael H. Perrott

Broadband Communication System

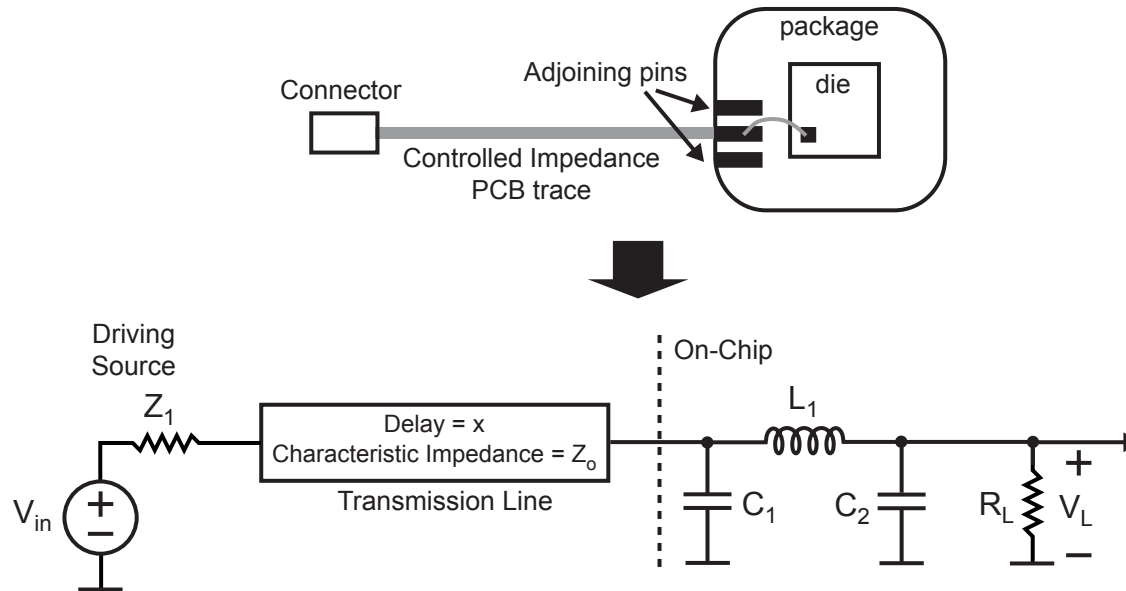
- Example: high speed data link on a PC board



- We've now studied how to analyze the transmission line effects and package parasitics
- What's next?





High Speed, Broadband Amplifiers

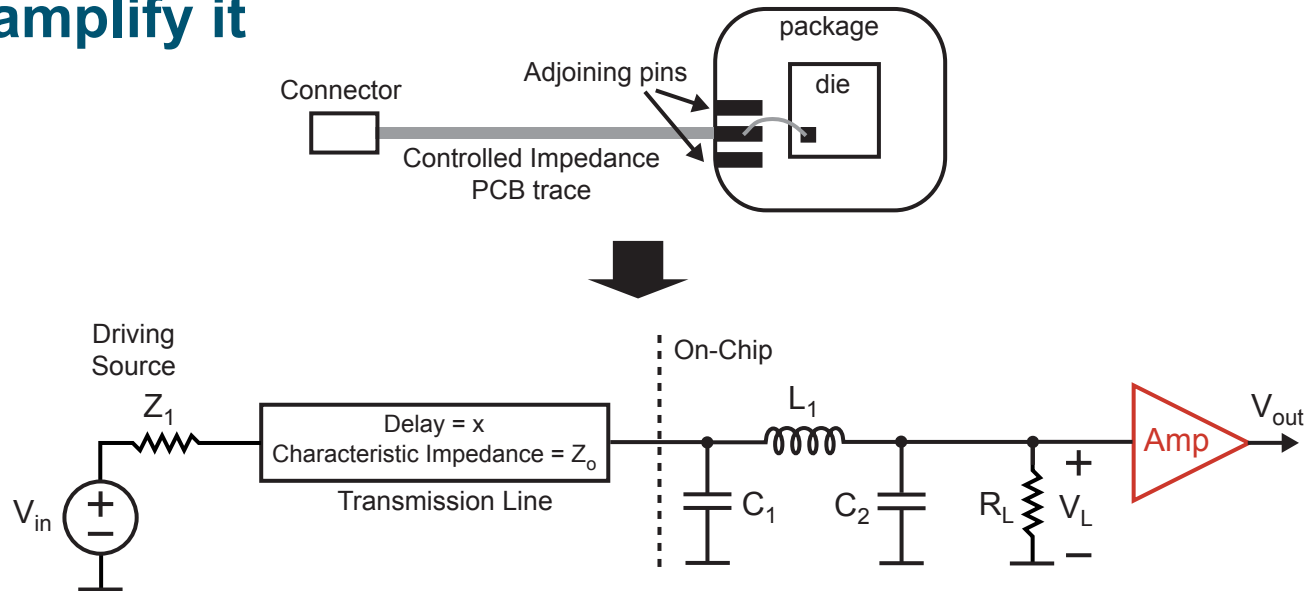- The first thing that you typically do to the input signal is amplify it




- **Function**
 - Boosts signal levels to acceptable values
 - Provides reverse isolation
- **Key performance parameters**
 - Gain, bandwidth, noise, linearity

    Basics of MOS Large Signal Behavior (Qualitative)



 
Basics of MOS Large Signal Behavior (Quantitative)



$$I_{\text{D}} = \mu_{\text{n}} C_{\text{ox}} \frac{W}{L} (V_{\text{GS}} - V_{\text{T}} - V_{\text{DS}}/2) V_{\text{DS}}$$


for $V_{\text{DS}} \ll V_{\text{GS}} - V_{\text{T}}$
 
$$I_{\text{D}} \approx \mu_{\text{n}} C_{\text{ox}} \frac{W}{L} (V_{\text{GS}} - V_{\text{T}}) V_{\text{DS}}$$



$$\Delta V = V_{\text{GS}} - V_{\text{T}}$$
 
$$\Delta V = \sqrt{\frac{2I_{\text{D}}L}{\mu_{\text{n}}C_{\text{ox}}W}}$$




$$I_{\text{D}} = \frac{1}{2} \mu_{\text{n}} C_{\text{ox}} \frac{W}{L} (V_{\text{GS}} - V_{\text{T}})^2 (1 + \lambda V_{\text{DS}})$$

(where λ corresponds to channel length modulation)

Analysis of Amplifier Behavior

 - Typically focus on small signal behavior
 - Work with a linearized model such as hybrid- π
 - Thevenin modeling techniques allow fast and efficient analysis
- To do small signal analysis:




Small Signal Analysis Steps

- 1) Solve for bias current I_D
- 2) Calculate small signal parameters (such as g_m , r_o)
- 3) Solve for small signal response using transistor hybrid- π small signal model


MOS DC Small Signal Model

- Assume transistor in saturation:

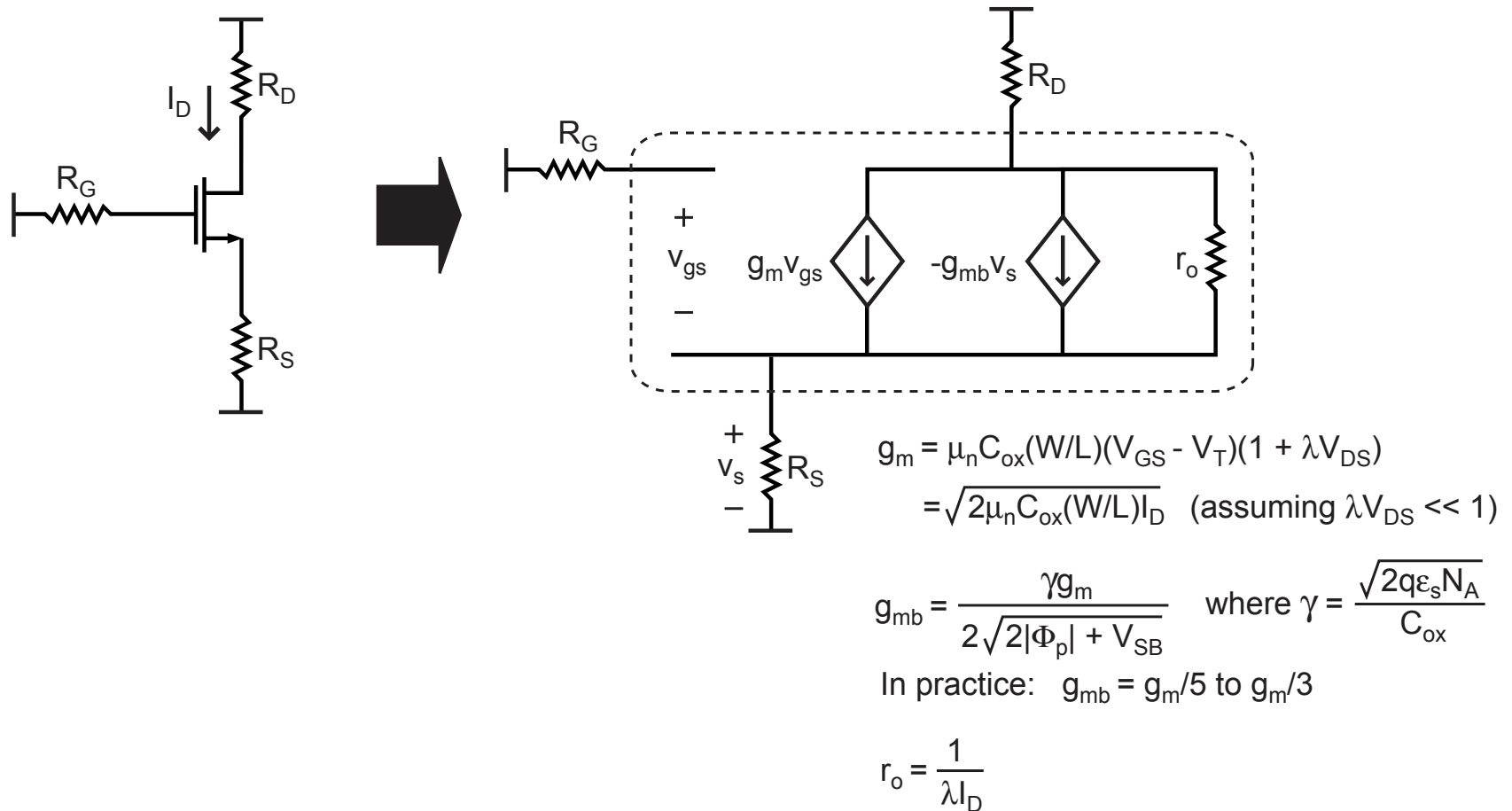

- Thevenin modeling based on the above

Capacitors For MOS Device In Saturation

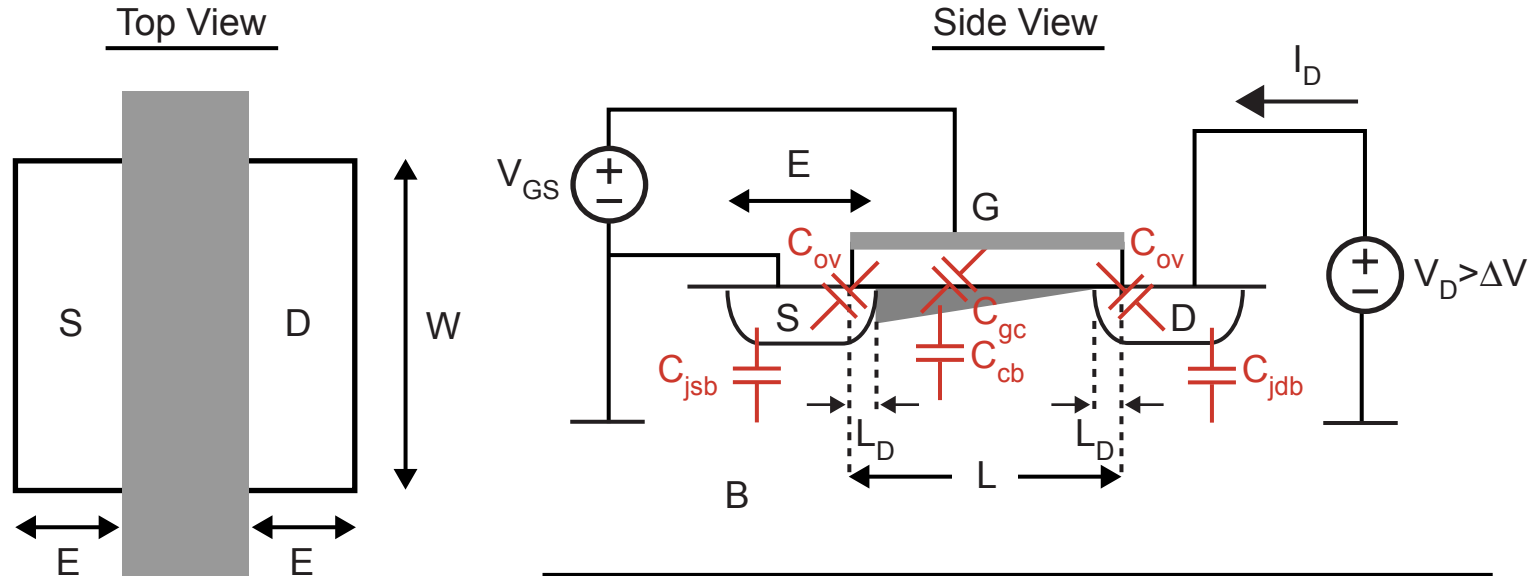

junction bottom wall
cap (per area)

junction sidewall
cap (per length)

$$\text{source to bulk cap: } C_{jsb} = \frac{C_j(0)}{\sqrt{1 + V_{SB}/|\Phi_B|}} WE + \frac{C_{jsw}(0)}{\sqrt{1 + V_{SB}/|\Phi_B|}} (W + 2E)$$


$$\text{drain to bulk cap: } C_{jdb} = \frac{C_j(0)}{\sqrt{1 + V_{DB}/|\Phi_B|}} WE + \frac{C_{jsw}(0)}{\sqrt{1 + V_{DB}/|\Phi_B|}} (W + 2E)$$

(make 2W for "4 sided" perimeter in some cases)

$$\text{overlap cap: } C_{ov} = WL_D C_{ox} + WC_{fringe} \quad \text{gate to channel cap: } C_{gc} = \frac{2}{3} C_{ox} W(L - 2L_D)$$

channel to bulk cap: C_{cb} - ignore in this class

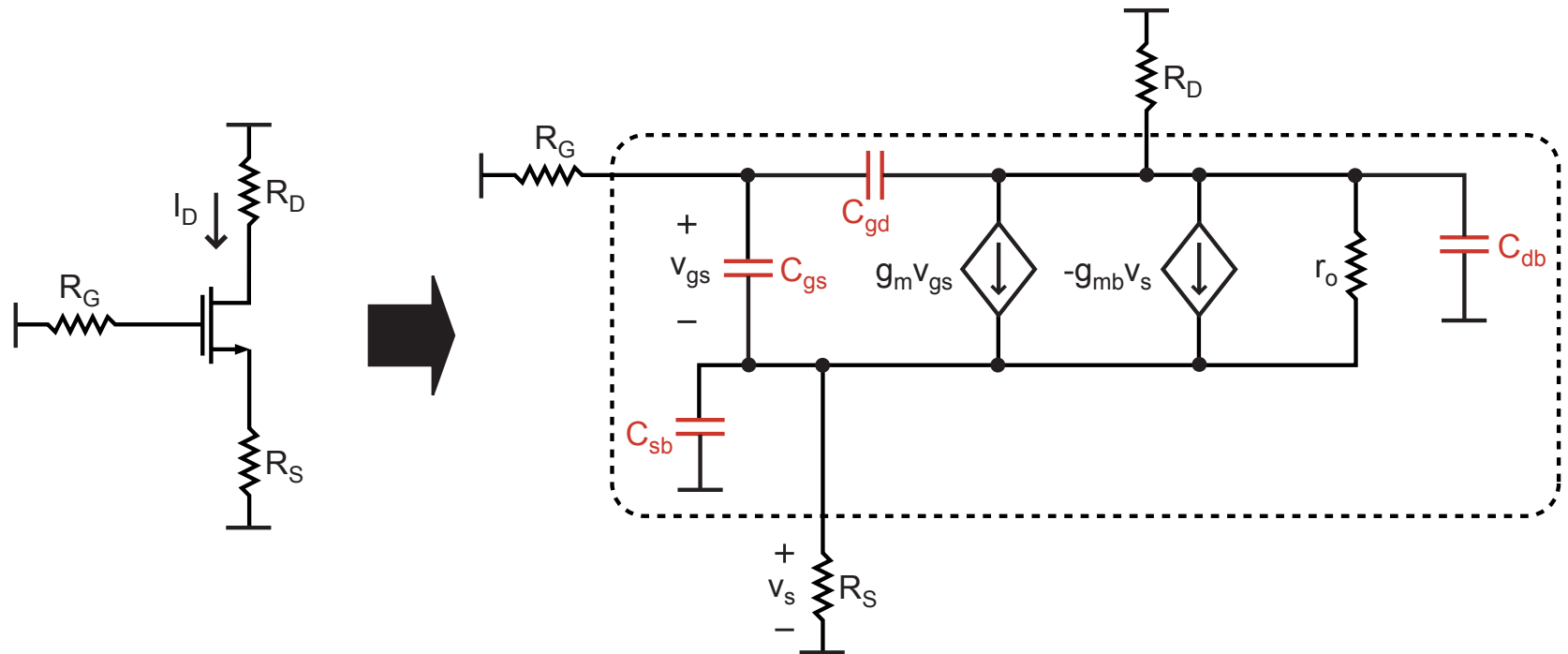MOS AC Small Signal Model (Device in Saturation)



$$C_{gs} = C_{gc} + C_{ov} = \frac{2}{3} C_{ox} W(L-2L_D) + C_{ov}$$

$$C_{gd} = C_{ov}$$

$$C_{sb} = C_{jsb} \quad (\text{area + perimeter junction capacitance})$$

$$C_{db} = C_{jdb} \quad (\text{area + perimeter junction capacitance})$$

Wiring Parasitics

■ Capacitance

- Gate: cap from poly to substrate and metal layers
- Drain and source: cap from metal routing path to substrate and other metal layers

■ Resistance

- Gate: poly gate has resistance (reduced by silicide)
- Drain and source: some resistance in diffusion region, and from routing long metal lines

■ Inductance


- Gate: poly gate has negligible inductance
- Drain and source: becoming an issue for long wires

Extract these parasitics from circuit layout

Frequency Performance of a CMOS Device


- **Two figures of merit in common use**
 - f_t : frequency for which current gain is unity
 - f_{\max} : frequency for which power gain is unity
- **Common intuition about f_t**
 - **Gain, bandwidth product is conserved**
$$\Rightarrow \text{Gain} \cdot \text{Bandwidth} = f_t$$
 - **We will see that MOS devices have an f_t that shifts with bias**
 - This effect strongly impacts high speed amplifier topology selection
- **We will focus on f_t**
 - **Look at pages 70-72 of Tom Lee's book for discussion on f_{\max}**

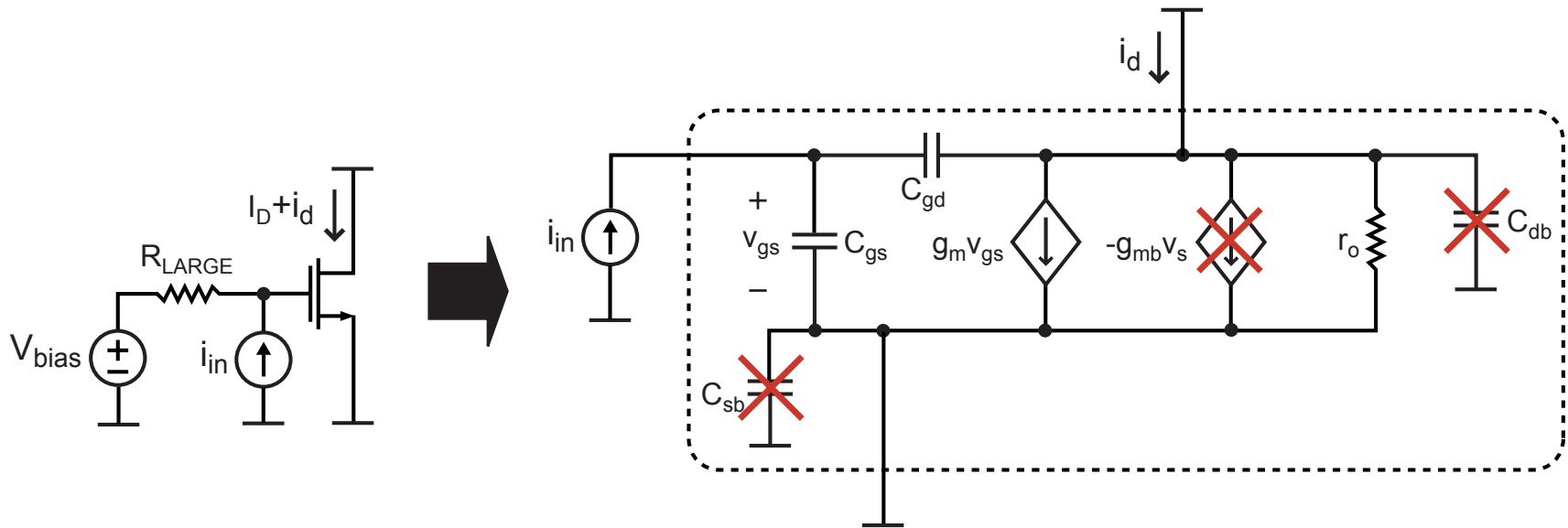Derivation of f_t for MOS Device in Saturation



- Assumption is that input is current, output of device is short circuited to a supply voltage
 - Note that voltage bias is required at gate
 - The calculated value of f_t is a function of this bias voltage

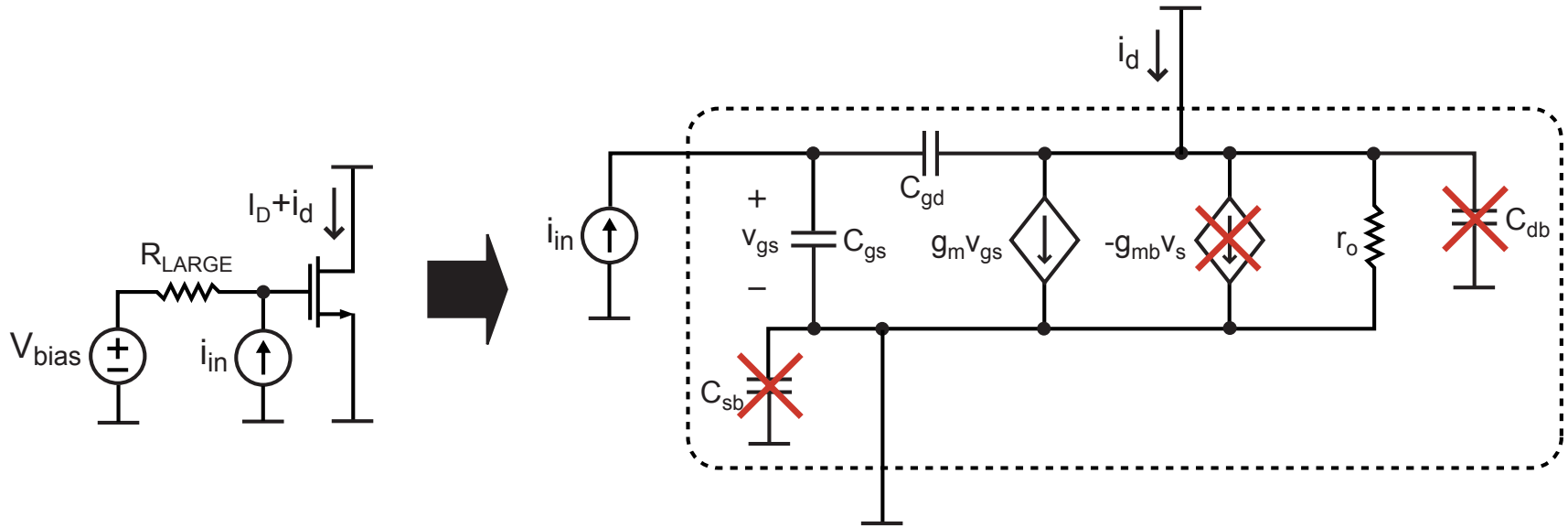
Derivation of f_t for MOS Device in Saturation



$$i_d = g_m v_{gs} = g_m \left(\frac{1}{s(C_{gs} + C_{gd})} \right) i_{in}$$

$$\Rightarrow \frac{i_d}{i_{in}} = \frac{g_m}{j2\pi f(C_{gs} + C_{gd})}$$

 Derivation of f_t for MOS Device in Saturation



$$\Rightarrow f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$i_d = g_m v_{gs} = g_m \left(\frac{1}{s(C_{gs} + C_{gd})} \right) i_{in}$$

$$\Rightarrow \frac{i_d}{i_{in}} = \frac{g_m}{j2\pi f(C_{gs} + C_{gd})}$$

Why is f_t a Function of Voltage Bias?

$$f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- f_t is a ratio of g_m to gate capacitance
 - g_m is a function of gate bias, while gate cap is not (so long as device remains biased)
- First order relationship between g_m and gate bias:

$$g_m \approx \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)$$

- The larger the gate bias, the higher the value for f_t
- Alternately, f_t is a function of current density

$$\frac{g_m}{C_{gs} + C_{gd}} \approx \frac{\sqrt{2\mu_n C_{ox} (W/L) I_d}}{(2/3)WLC_{ox} + W(C_{ov}/W)} \propto \sqrt{\frac{I_d}{W}}$$

- So f_t maximized at max current density (and minimum L)

Speed of NMOS Versus PMOS Devices

$$f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- **NMOS devices have much higher mobility than PMOS devices (in current, non-strained, bulk CMOS processes)**


$$\mu_n \approx 2.5\mu_p \quad \text{for many processes}$$

$$\Rightarrow f_t \text{ of NMOS} \approx 2.5 \times f_t \text{ of PMOS}$$

- **Intuition: NMOS devices provide approximately $2.5 \times g_m$ for a given amount of capacitance and gate bias voltage**
- **Also: NMOS devices provide approximately $2.5 \times I_d$ for a given amount of capacitance and gate bias voltage**

Assumptions for High Speed Amplifier Analysis

 
- Assume that amplifier is loaded by an identical amplifier and by fixed wiring capacitance



- Intrinsic performance
 - Defined as the bandwidth achieved for a given gain when C_{fixed} is negligible
 - Amplifier approaches intrinsic performance as its device sizes (and current) are increased
- In practice, optimal sizing (and power) of amplifier is roughly where $C_{in} + C_{out} = C_{fixed}$

The Miller Effect

 - Concerns impedances that connect from input to output of an amplifier



- Input impedance:**


$$Z_{in} = \frac{V_{in}}{(V_{in} - V_{out})/Z_f} = \frac{Z_f}{1 - A_v}$$

- Output impedance:**

$$Z_{out} = \frac{V_{out}}{(V_{out} - V_{in})/Z_f} = \frac{Z_f}{1 - 1/A_v} \approx Z_f \text{ for } |A_v| \gg 1$$

 Example: The Impact of Capacitance in Feedback

- Consider C_{gd} in the MOS device as C_f
 - Assume gain is negative



- Impact on input capacitance:


$$Z_{in} = \frac{1/(sC_f)}{1 + |A_v|} = \frac{1}{sC_f(1 + |A_v|)} \Rightarrow \text{looks like larger cap!}$$

- Output impedance:

$$Z_{out} = \frac{1/(sC_f)}{1 + 1/|A_v|} = \frac{1}{sC_f(1 + 1/|A_v|)} \Rightarrow \text{only slightly larger!}$$

Amplifier Example – CMOS Inverter

 
- Assume that we set V_{bias} such that the amplifier nominal output is such that NMOS and PMOS transistors are all in saturation
 - Note: this topology VERY sensitive to bias errors




$$C_{\text{tot}} = C_{\text{db1}} + C_{\text{db2}} + C_{\text{gs3}} + C_{\text{gs4}} + K(C_{\text{ov3}} + C_{\text{ov4}}) + C_{\text{fixed}}$$

(+ $C_{\text{ov1}} + C_{\text{ov2}}$) Miller multiplication factor

Transfer Function of CMOS Inverter

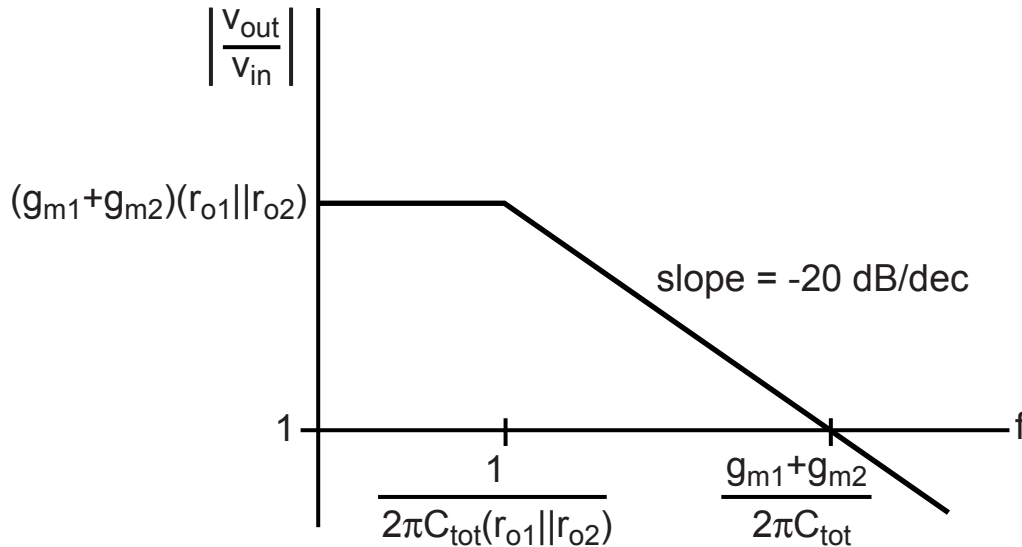


Low Bandwidth!

 


$$C_{tot} = C_{db1} + C_{db2} + C_{gs3} + C_{gs4} + K(C_{ov3} + C_{ov4}) + C_{fixed}$$

\uparrow
 $(+C_{ov1} + C_{ov2})$ Miller multiplication factor

Add Resistive Feedback

 

 Bandwidth extended and less sensitivity to bias offset




$$C_{tot} = C_{db1} + C_{db2} + C_{gs3} + C_{gs4} + K(C_{ov3} + C_{ov4}) + C_{Rf}/2 + C_{fixed}$$

$(+C_{ov1} + C_{ov2})$ Miller multiplication factor

We Can Still Do Better

 - We are fundamentally looking for high g_m to capacitance ratio to get the highest bandwidth
 - PMOS degrades this ratio
 - Gate bias voltage is constrained




$$C_{tot} = C_{db1} + C_{db2} + C_{gs3} + C_{gs4} + K(C_{ov3} + C_{ov4}) + C_{Rf}/2 + C_{fixed}$$

↑
↑

(+C_{ov1} + C_{ov2})
Miller multiplication factor

Take PMOS Out of the Signal Path

 


■ Advantages

- PMOS gate no longer loads the signal
- NMOS device can be biased at a higher voltage

■ Issue

- PMOS is not an efficient current provider (I_d /drain cap)
 - Drain cap close in value to C_{gs}
- Signal path is loaded by cap of R_f and drain cap of PMOS

Shunt-Series Amplifier

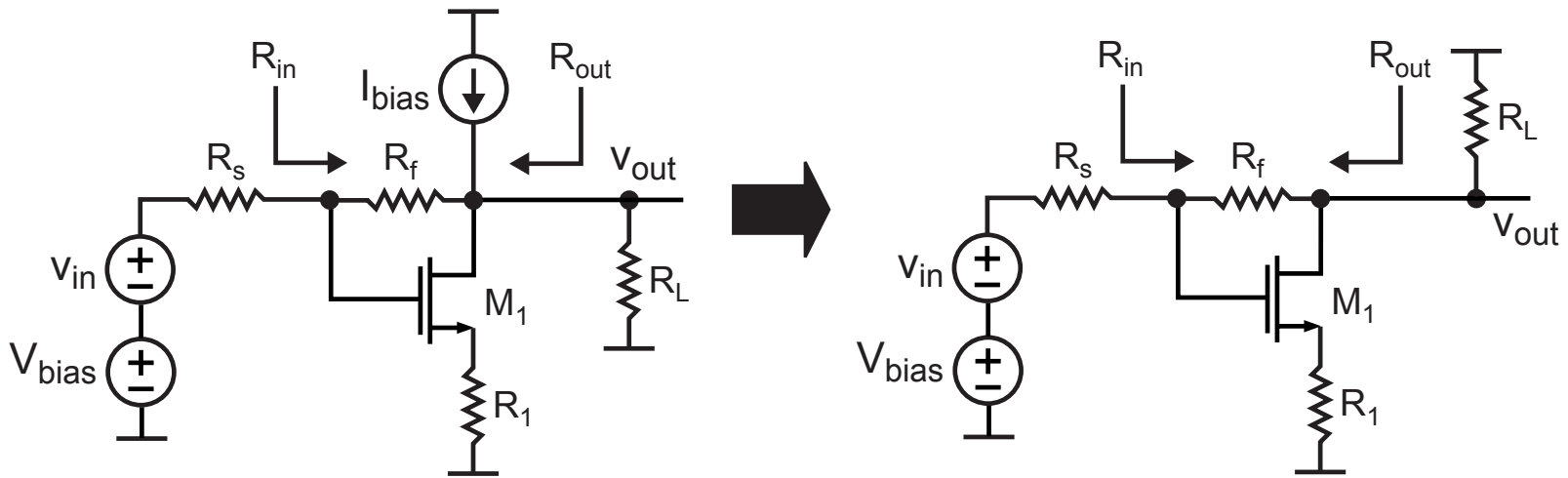

- **Use resistors to control the bias, gain, and input/output impedances**
 - Improves accuracy over process and temp variations
- **Issues**
 - Degeneration of M_1 lowers slew rate for large signal applications (such as limit amps)
 - There are better high speed approaches – the advantage of this one is simply accuracy


Shunt-Series Amplifier – Analysis Snapshot

- From Chapter 8 of Tom Lee's book (see pp 191-197):

- Gain

$$A_v = \frac{v_{out}}{v_{in}} = -\frac{R_L}{R_E} \left(\frac{R_f - R_E}{R_f + R_L} \right)$$

where: $R_E = 1/g_m + R_1$

 

Note: $A_v \approx -\frac{R_L}{R_1}$ for $R_f \gg R_L$, $R_f \gg R_E$, $R_1 \gg 1/g_m$

- Input resistance


$$R_{in} = \frac{R_f}{1 - A_v} = \frac{R_E(R_f + R_L)}{R_E + R_L} \approx \frac{R_f}{1 + R_L/R_1} \quad \text{for } R_f \gg R_L, R_1 \gg 1/g_m$$

- Output resistance

$$R_{out} = \frac{R_E(R_f + R_s)}{R_E + R_s} \approx \frac{R_f}{1 + R_s/R_1} \quad \text{for } R_f \gg R_s, R_1 \gg 1/g_m$$

Same for $R_s = R_L!$

NMOS Load Amplifier

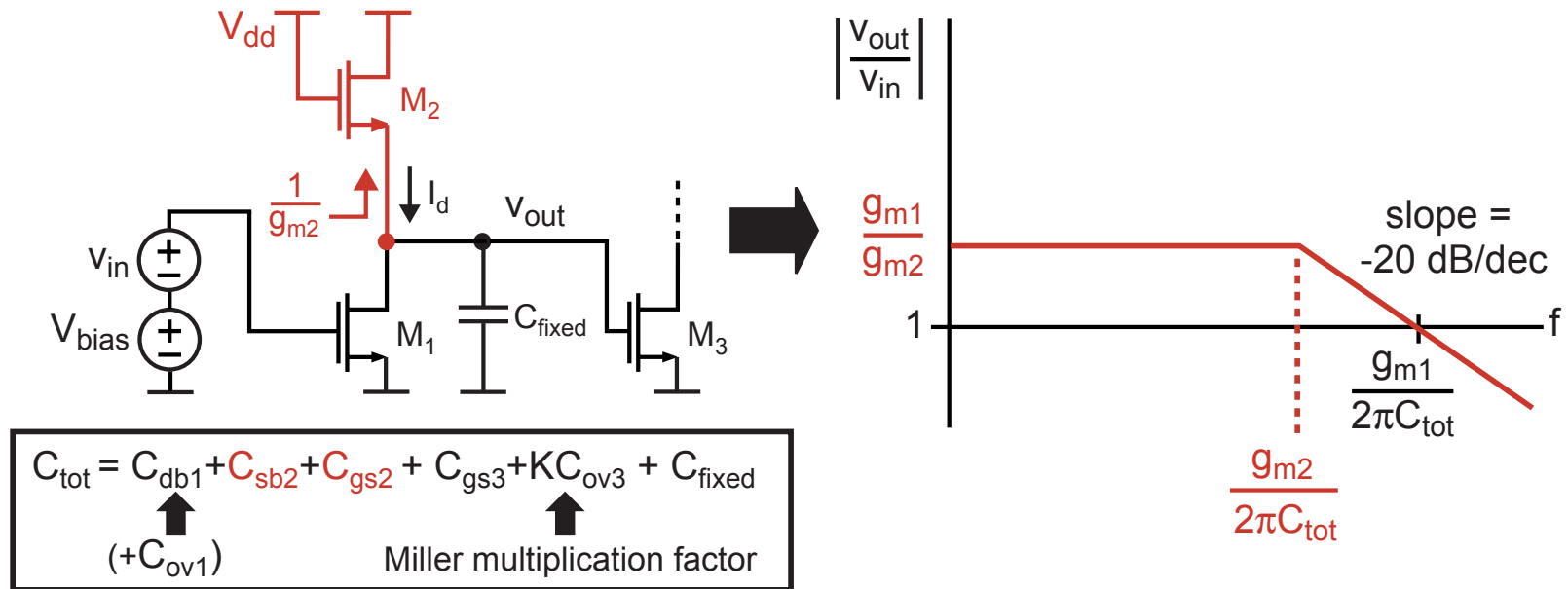

- Gain set by the relative sizing of M_1 and M_2

$$M_1 : I_{d1} = (1/2)\mu_n C_{ox} (W_1/L_1) (V_{IN} - V_T)^2$$


$$M_2 : I_{d2} = (1/2)\mu_n C_{ox} (W_2/L_2) (V_{dd} - V_{out} - V_T)^2 \quad \Rightarrow \quad I_{d1} = I_{d2}$$

$$\Rightarrow V_{out} = -AV_{IN} + V_{dd} + (A - 1)V_T$$

$$(V_{IN} = V_{in} + V_{bias})$$

$$\text{where } A = \sqrt{\frac{W_1/L_1}{W_2/L_2}}$$

Design of NMOS Load Amplifier

 


$$C_{\text{tot}} = \underset{\substack{\uparrow \\ (+C_{\text{ov}1})}}{C_{\text{db}1}} + C_{\text{sb}2} + C_{\text{gs}2} + C_{\text{gs}3} + \underset{\substack{\uparrow \\ \text{Miller multiplication factor}}}{KC_{\text{ov}3}} + C_{\text{fixed}}$$

$$A = \sqrt{\frac{W_1/L_1}{W_2/L_2}}$$

- **Size transistors for gain and speed**
 - Choose minimum L for maximum speed
 - Choose ratio of W_1 to W_2 to achieve appropriate gain
- **Problem: V_T of M_2 lowers the bias voltage of the next stage (thus lowering its achievable f_t)**
 - Severely hampers performance when amplifier is cascaded
 - One person solved this issue by increasing V_{dd} of NMOS load (see Sackinger et. al., “A 3-GHz 32-dB CMOS Limiting Amplifier for SONET OC-48 receivers”, JSSC, Dec 2000)

 
Resistor Loaded Amplifier (Unsilicided Poly)



- **This is the fastest non-enhanced amplifier I've found**
 - Unsilicided poly is a pretty efficient current provider (i.e., has a good current to capacitance ratio)
 - Output swing can go all the way up to V_{dd}
 - Allows following stage to achieve high f_t
 - **Linear settling behavior (in contrast to NMOS load)**

Implementation of Resistor Loaded Amplifier

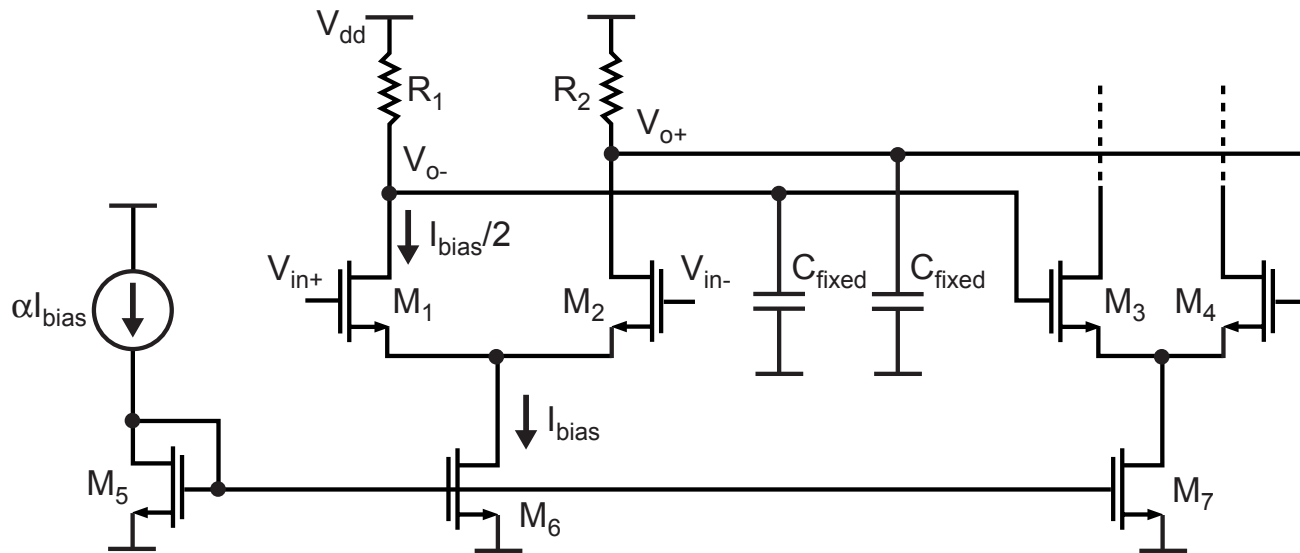- Typically implement using differential pairs



- Benefits
 - Self-biased
 - Common-mode rejection
- Negative
 - More power than single-ended version

The Issue of Velocity Saturation

- We classically assume that MOS current is calculated as

$$I_D = \frac{\mu_n C_{ox} W}{2 L} (V_{gs} - V_T)^2$$

- Which is really

$$I_D = \frac{\mu_n C_{ox} W}{2 L} (V_{gs} - V_T) V_{dsat,l}$$

- $V_{dsat,l}$ corresponds to the saturation voltage at a given length, which we often refer to as ΔV
- It may be shown that

$$V_{dsat,l} \approx \frac{(V_{gs} - V_T)(LE_{sat})}{(V_{gs} - V_T) + (LE_{sat})} = (V_{gs} - V_T) \parallel (LE_{sat})$$

- If $V_{gs} - V_T$ approaches LE_{sat} in value, then the top equation is no longer valid
 - We say that the device is in velocity saturation

Analytical Device Modeling in Velocity Saturation

- If L small (as in modern devices), then velocity saturation will impact us for even moderate values of $V_{gs} - V_T$

$$I_D = \frac{\mu_n C_{ox} W}{2 L} (V_{gs} - V_T) [(V_{gs} - V_T) \parallel (L E_{sat})]$$



$$\Rightarrow I_D \approx \frac{\mu_n C_{ox}}{2} W (V_{gs} - V_T) E_{sat}$$

- Current increases linearly with $V_{gs} - V_T$!
- Transconductance in velocity saturation:



$$g_m = \frac{dI_d}{dV_{gs}} \Rightarrow g_m = \frac{\mu_n C_{ox}}{2} W E_{sat}$$

- No longer a function of V_{gs} !

  
Example: Current Versus Voltage for 0.18μ Device



  Example: G_m Versus Voltage for 0.18μ Device




 Example: G_m Versus Current Density for 0.18μ Device



Note: $I_{den} = \frac{I_d}{W} = \frac{I_d}{1.8\mu}$

Transconductance versus Current Density

 

How Do We Design the Amplifier?


- Highly inaccurate to assume square law behavior
- We will now introduce a numerical procedure based on the simulated g_m curve of a transistor
 - A look at g_m assuming square law device:

$$g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_d} = W \sqrt{2\mu C_{ox} \frac{W}{L} \left(\frac{I_d}{W}\right)}$$

- Observe that if we keep the current density (I_d/W) constant, then g_m scales directly with W
 - This turns out to be true outside the square-law regime as well
- We can therefore relate g_m of devices with different widths given that have the same current density

$$g_m(W, I_{den}) = \frac{W}{W_o} g_m(W_o, I_{den})$$

 A Numerical Design Procedure for Resistor Amp – Step 1



■ Two key equations

- Set gain and swing (single-ended)

$$(1) \quad g_m(W, I_{bias}/W)R = A$$

$$(2) \quad V_{sw} = 2I_{bias}R$$

■ Equate (1) and (2) through R

$$\frac{A}{g_m(W, I_{bias}/W)} = \frac{V_{sw}}{2I_{bias}}$$

$$\Rightarrow g_m(W, I_{bias}/W) = 2 \frac{A}{V_{sw}} W \left(\frac{I_{bias}}{W} \right)$$

Can we relate this formula to a g_m curve taken from a device of width W_o ?

A Numerical Design Procedure for Resistor Amp – Step 2

- We now know:

$$(1) \quad g_m(W, I_{bias}/W) = 2 \frac{A}{V_{sw}} W \left(\frac{I_{bias}}{W} \right)$$

$$(2) \quad g_m(W, I_{den}) = \frac{W}{W_o} g_m(W_o, I_{den})$$

- Substitute (2) into (1)

$$\frac{W}{W_o} g_m(W_o, I_{bias}/W) = 2 \frac{A}{V_{sw}} W \left(\frac{I_{bias}}{W} \right)$$


$$\Rightarrow g_m(W_o, I_{den}) = 2 W_o \frac{A}{V_{sw}} I_{den}$$

- The above expression allows us to design the resistor loaded amp based on the g_m curve of a representative transistor of width W_o !

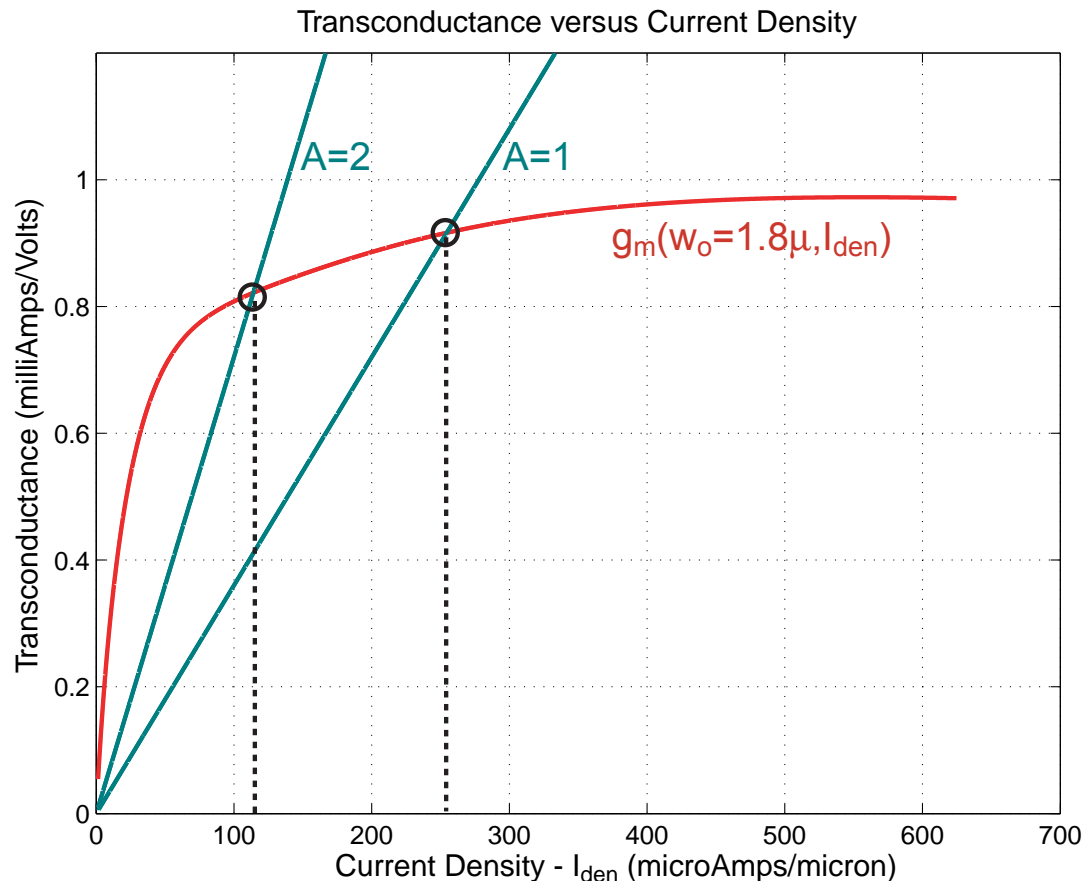Example: Design for Swing of 1 V, Gain of 1 and 2

$$g_m(W_o, I_{den}) = 2W_o \frac{A}{V_{sw}} I_{den}$$

- Assume $L=0.18\mu$, use previous g_m plot ($W_o=1.8\mu$)



- For gain of 1, current density = $250 \mu\text{A}/\mu\text{m}$
- For gain of 2, current density = $115 \mu\text{A}/\mu\text{m}$
- Note that current density reduced as gain increases!
 - f_t effectively decreased

Example (Continued)


- Knowledge of the current density allows us to design the amplifier
 - Recall $V_{sw} = 2I_{bias}R$
 - Free parameters are W , I_{bias} , and R (L assumed to be fixed)
- Given $I_{den} = 115 \mu\text{A}/\mu\text{m}$ (Swing = 1V, Gain = 2)
 - If we choose $I_{bias} = 300 \mu\text{A}$

$$I_{den} = \frac{I_{bias}}{W} \Rightarrow W = \frac{300}{115} = 2.6 \mu\text{m}$$

$$V_{sw} = 2I_{bias}R \Rightarrow R = \frac{1}{2 \cdot 300 \times 10^{-6}} = 1.67 \text{k}\Omega$$

- Note that we could instead choose W or R , and then calculate the other parameters

 How Do We Choose I_{bias} For High Bandwidth?



- As you increase I_{bias} , the size of transistors also increases to keep a constant current density
 - The size of C_{in} and C_{out} increases relative to C_{fixed}
- To achieve high bandwidth, want to size the devices (i.e., choose the value for I_{bias}), such that
 - $C_{in} + C_{out}$ roughly equal to C_{fixed}